 


Sequential Circuits: Latches and Flip-Flops

Sequential circuits

- Output depends on current input *and* past sequence of input(s)
- How can we tell if the input is current or from the past?
- A clock pulse can cause **state changes** in sequential circuits.




- What about an active low clock, i.e. CLK_L?
- Sequential circuits can **remember** past inputs
 - “**Memory**” is needed to remember the past

Practical discrete designs

- Feedback sequential circuits
 - Use ordinary gates and feedback loops to obtain memory in a logic circuit
 - Thus creating sequential-circuit building blocks, e.g. latches and flip-flops (many kinds)
- Clocked synchronous state machines
 - Use the building blocks from above, esp. edge-triggered D flip-flops, to create sequential circuits
 - Whose inputs are examined and whose outputs change according to a controlling clock signal (the “triggering”)


Bistable element

 - Simplest sequential circuit – 2 inverters forming a feedback loop
- Has two states
 - 1 state variable, Q , represents 2 states, i.e. $Q = 0$ and $Q = 1$




Bistable element

 - Simplest sequential circuit – 2 inverters forming a feedback loop
- Has two states
 - 1 state variable, Q , represents 2 states, i.e. $Q = 0$ and $Q = 1$




Analog analysis

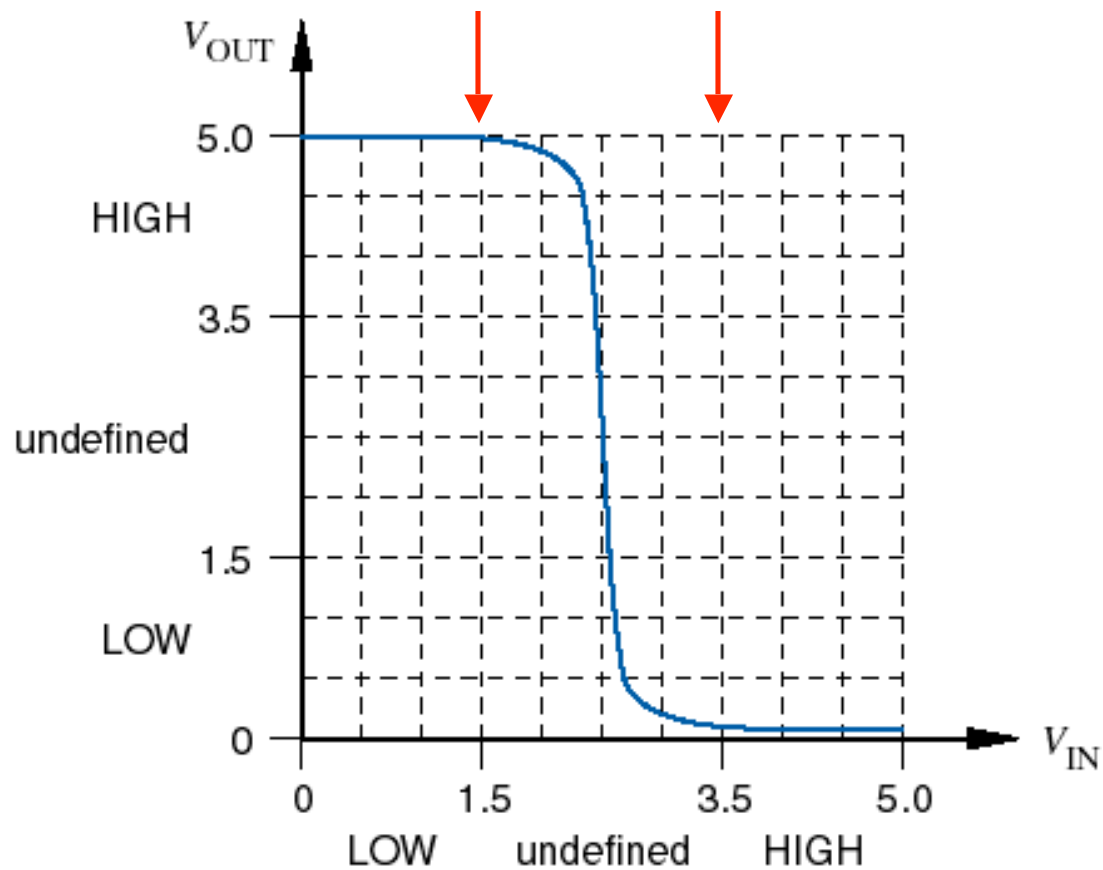- Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V



Analog analysis

 
- Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V




- Q and Q_L are not valid at 2.5 V.
- But in theory they can stay as such indefinitely – metastable!

Analog analysis

 - Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V




In metastable state

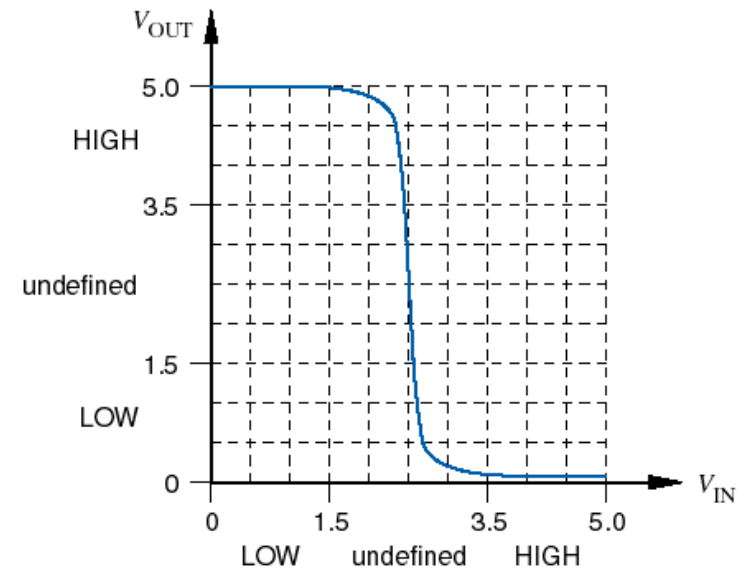

Metastability

 - Metastability is inherent in a bistable element




Transfer function:

$$V_{out1} = T(V_{in1})$$



$$V_{out2} = T(V_{in2})$$

 - Two stable points, one metastable point



Control the inputs for the bistable element?

  - How do we control its inputs?
 - Add **control inputs** S and R
- Now we have an **S-R latch**
- When $S=R=0$, Q “stores” the last Q (**S: set, R: reset**)
- 2 NOR gates are used




S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

S-R latch operation


- When $S=R=0$, the latch behaves like a **bistable element**
 - Because $(x+0)' = x' \cdot 0' = x' \cdot 1 = x'$
- When $S=R=1$, we have both Q and QN equal to 0
 - Because $(x+1)' = x' \cdot 1' = x' \cdot 0 = 0$
- Abnormal state for S-R latch is reached when $S=R=1$
 - Because $Q=QN=0$, but Q should \neq QN , logically
- Can you trace the remaining rows of the **function table**?
 - That is, when $(S=0, R=1)$ and $(S=1, R=0)$, what are Q and QN?

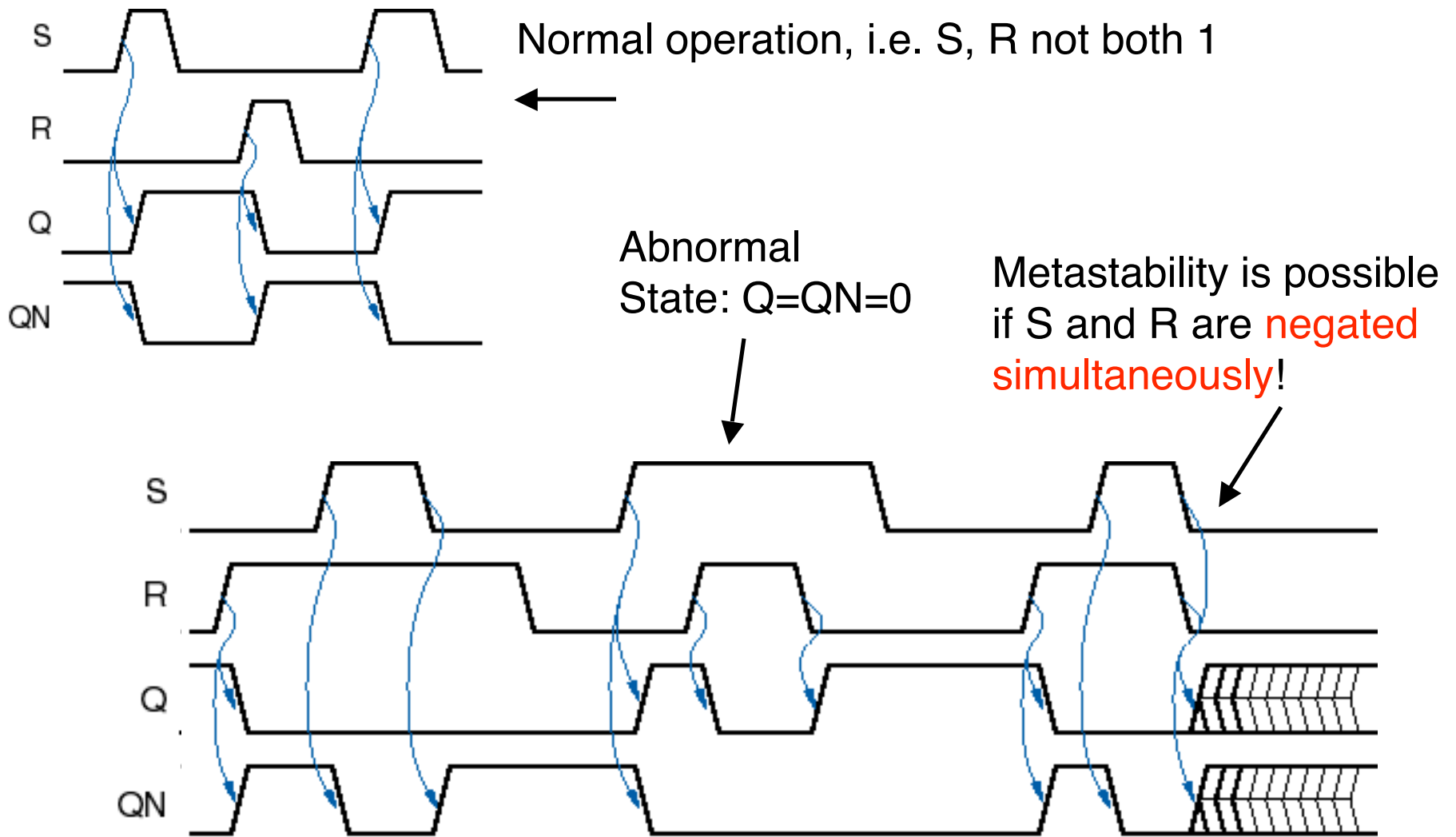S-R latch operation (blue arrows indicate causality)





S-R latch timing parameters


 
- Propagation delay, e.g. LO-HI transition on S causes LO-HI on Q
- Minimum pulse width, $t_{pw(min)}$: **minimum** duration for an S (or R) transition to cause a “stable” transition of Q
- Latch remains metastable for a random duration of time
- Wait for **at least** $t_{pw(min)}$ after asserting S/R to avoid metastability



S-R latch symbols

 
 


Preferred symbol

  

What's this?!

  S-R latch using NAND gates (a.k.a. S-bar-R-bar latch)



- S and R are active-low (not Q/QN)
- Can be built with NAND gates
- Much more popular than NOR logic
- Because NAND is faster than NOR
- Abnormal state: $S_L = R_L = 0$

S_L	R_L	Q	Q_N
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last Q_N

S-R latch with enable (a.k.a. gated/clocked S-R latch)


S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

Let C decide whether S and R can result in a bistable element.

C can be a clock signal!



Now S and R are active-high again.

 Metastability occurs when S=R=1, and C transitions from 1 to 0.



D latch (D for Data)


C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

  

S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

Think of this as a gated S-R latch with $R=S'$ \Rightarrow Only 3 rows of the FT remain.

D latch operation

 


When $C = 1$, $Q = D$, i.e. Q “follows” D

When $C = 0$, Q does not change, i.e. Q “stores” the last D

D latch is (clock) level-triggered, not edge-triggered

D latch timing parameters

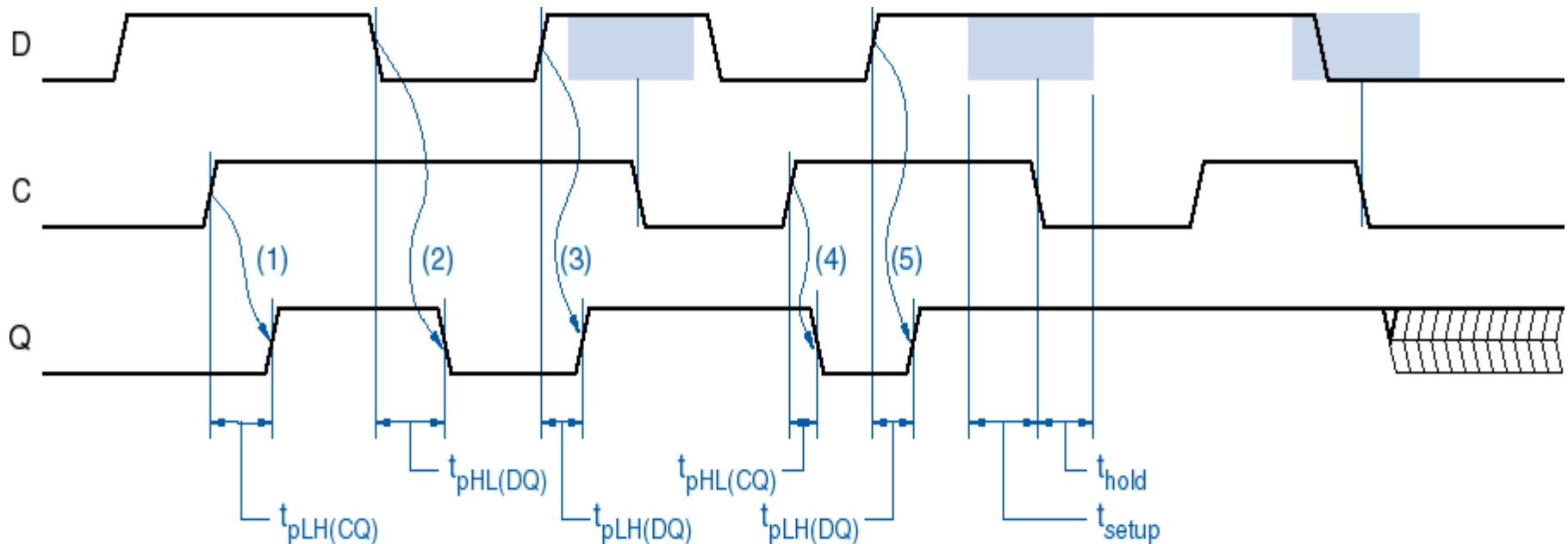
- When $C = 1$, Q follows D with delay
 - Propagation delays (in Q caused by C or D), i.e. $t_{pLH(**)}$ and $t_{pHL(**)}$
- When $C = 0$, Q remembers D during C 's $1 \rightarrow 0$ transition
 - Setup time (D before C 's falling edge), i.e. t_{setup}
 - Hold time (D after C 's falling edge), i.e. t_{hold}
 - If D does not remain the same for $> (t_{setup} + t_{hold}) \Rightarrow$ metastability!




Positive edge-triggered D flip-flop (uses 2 D latches)

	D	CLK	Q	QN
1	0		0	1
2	1		1	0
3	x	0	last Q	last QN
4	x	1	last Q	last QN

- Row 1: M closed, S open, $Q = QM = D = 0$
- Row 2: M closed, S open, $Q = QM = D = 1$
- Row 3: M open and follows D, S closed
- Row 4: S open and follows QM, M closed
 - Row 1/2: M open \rightarrow close, S close \rightarrow open
 - Row 3 and Row 4 keep the **last Q** and **QN**
- S is open while $CLK=1$, but only changes at the beginning of this interval, because M is closed (unchanged) during rest of interval.
- Q only changes during CLK transitions

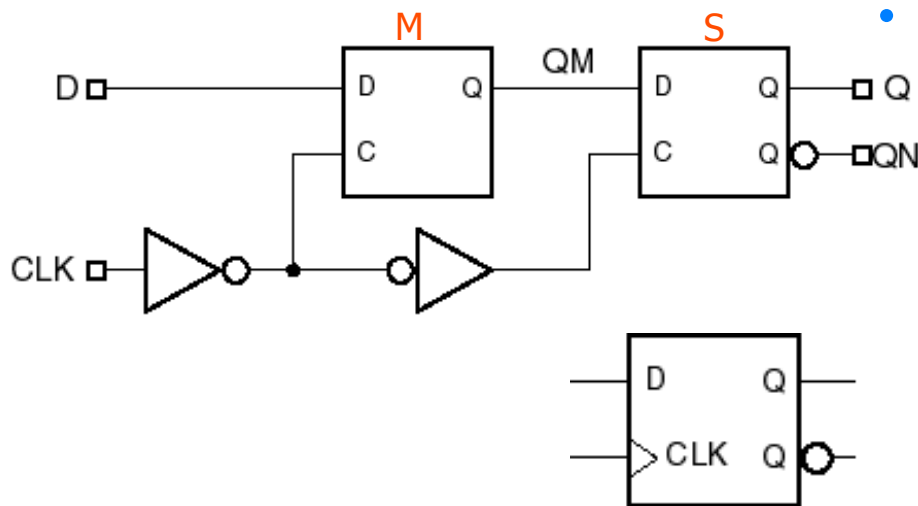


C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

 

D latch

 
Positive edge-triggered D flip-flop functional behavior



CLK (f/ M)	CLK_L (f/ S)	Latch M status	QM	Latch S status	Q
1	0	closed	$D_{last}@ \uparrow$	open	QM =
↓	↑	closed → open	$D_{last}@ \uparrow$	open → closed	$D_{last}@ \uparrow$
0	1	open	D (QM)	closed	$D_{last}@ \uparrow$
↑	↓	open → closed	D	closed → open	$D_{last}@ \uparrow$
1	0	closed	$D@ \uparrow$	open	QM = $D@ \uparrow$



D flip-flop timing parameters

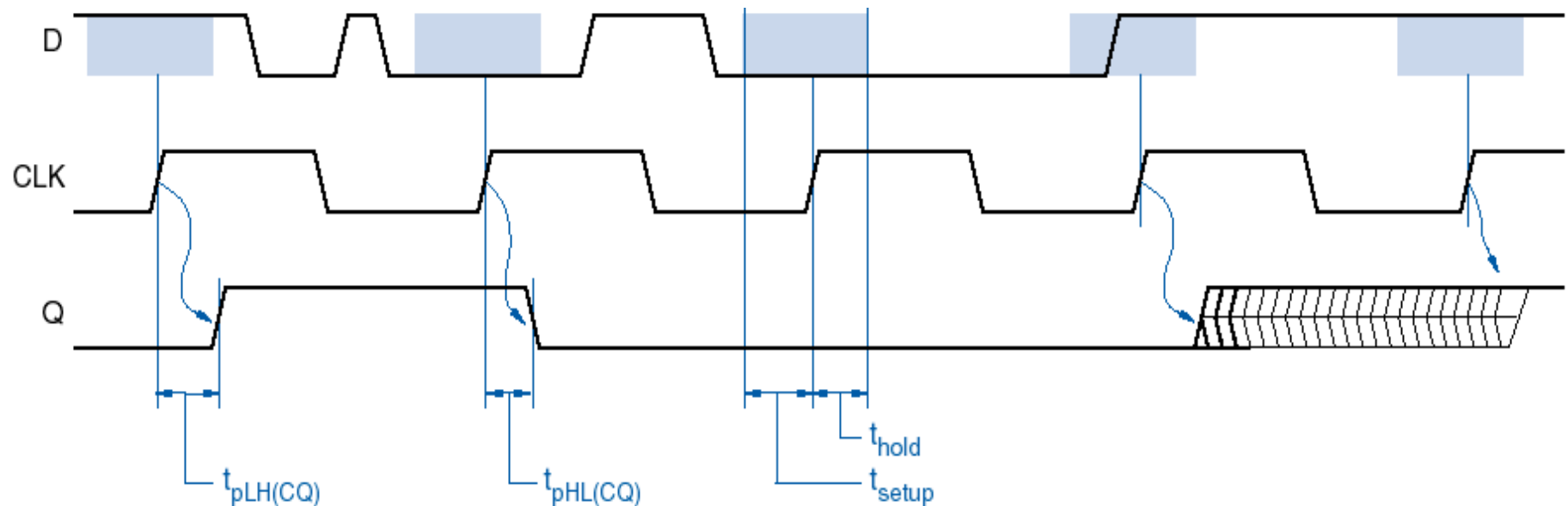- Propagation delay (from CLK threshold to Q threshold, i.e. “CQ”)
- Setup time (D before CLK)
- Hold time (D after CLK)
- D must not change within (Setup + Hold) window
- Window occurs around the triggering edge of CLK




Positive edge-triggered D flip-flop with Preset and Clear

  - Preset and clear inputs
 - Works like S-R latch



Negative edge-triggered D flip-flop

- Invert the input CLK signal

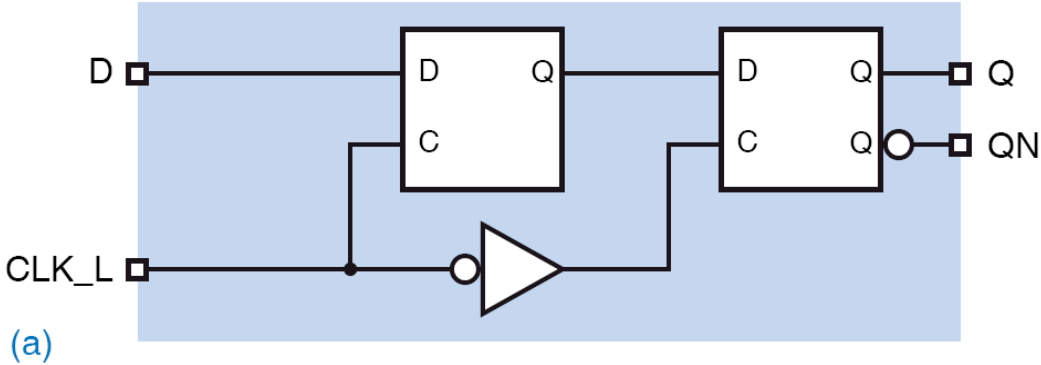


D	CLK	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN

(a)

D	CLK_L	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN


(b)

 

(c)

+ve edge-triggered D FF

 
Positive-edge-triggered D flip-flop with enable




EN = 1: D = external D
 EN = 0: D = last Q
 CLK = 0/1: keep last Q

(b)

D	EN	CLK	Q	QN
0	1		0	1
1	1		1	0
x	0		last Q	last QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN

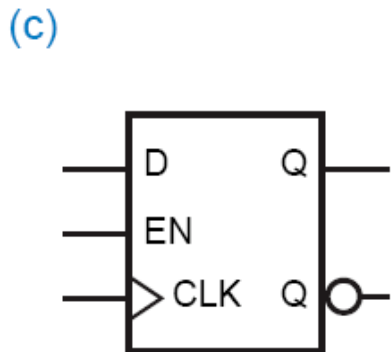


Edge-Triggered J-K flip-flop

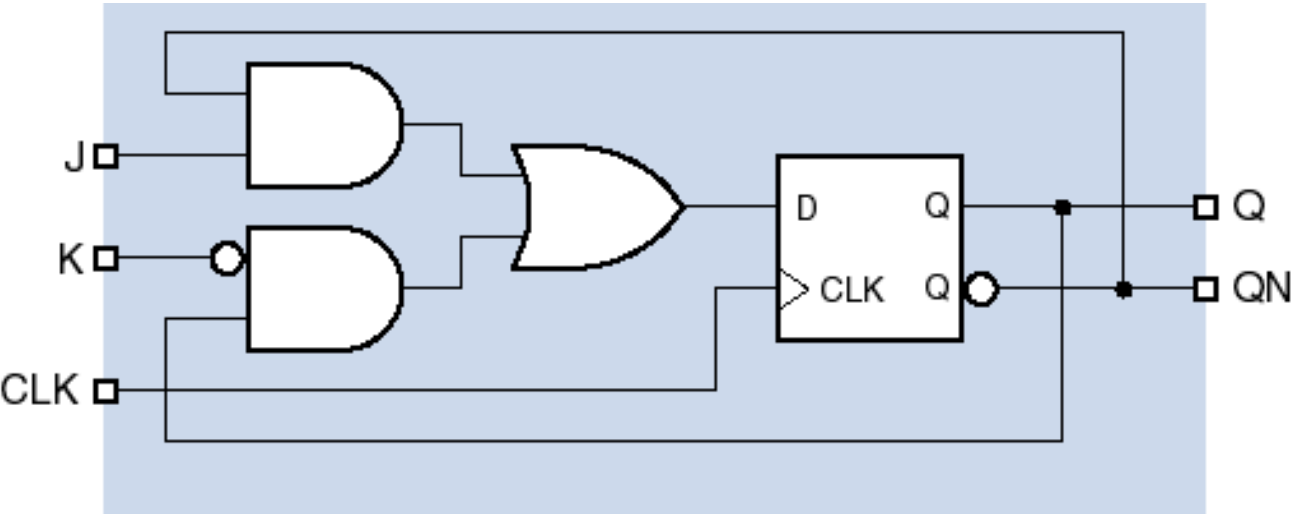


- Not used much anymore
- Don't worry about them


J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

 

 
Master/slave J-K flip-flop (pulse-triggered)




J	K	C	Q	QN
x	x	0	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

 

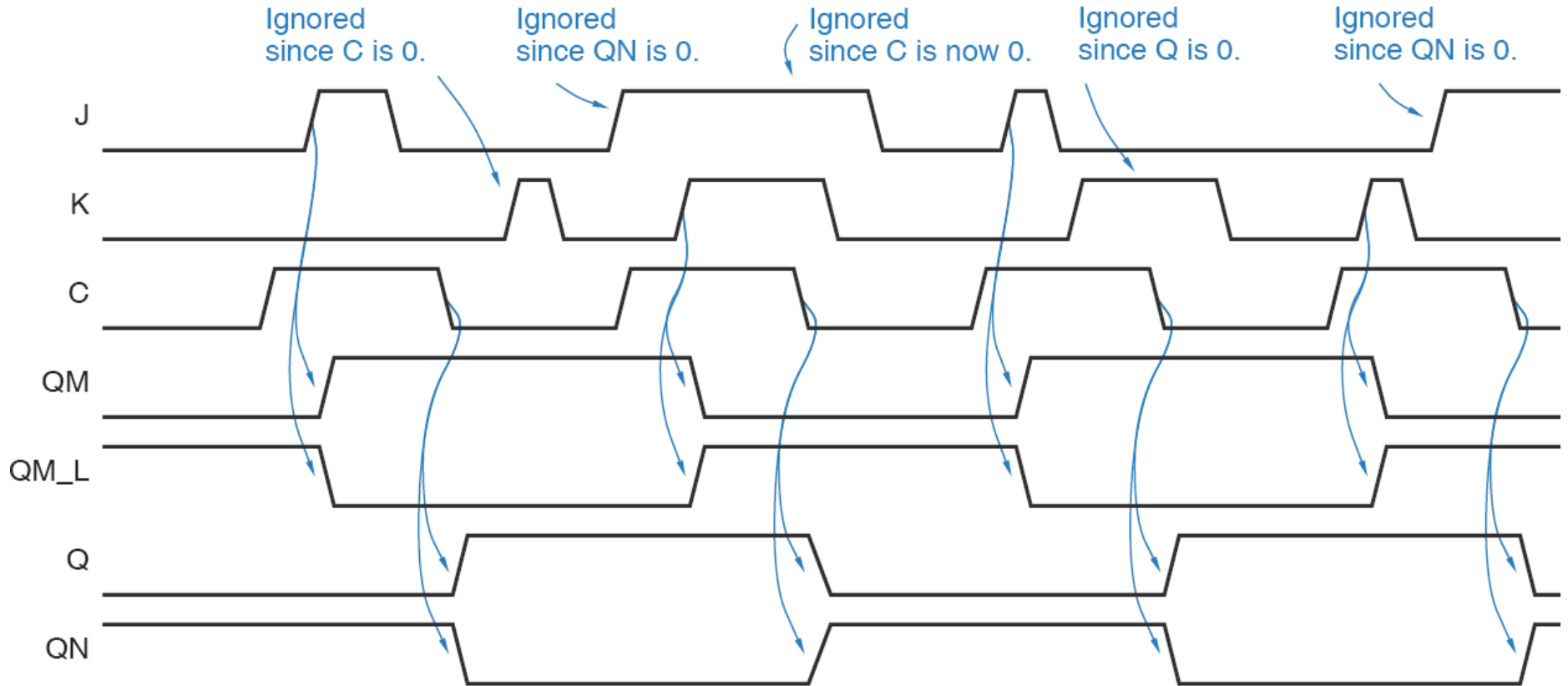
Timing diagram of master/slave J-K flip-flop







Master/slave S-R flip-flop

 

S	R	C	Q	QN
x	x	0	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		undef.	undef.




 


T flip-flops

    

T flip-flops with enable

- Important for counters

    

Many types of latches and flip-flops

- S-R latch
- S_L-R_L latch
- S-R latch with enable
- D latch
- Edge-triggered D flip-flop
- Edge-triggered D flip-flop with enable
- Edge-triggered D flip-flop with preset and clear
- Scan flip-flop
- Edge-triggered J-K flip-flop
- Master/slave S-R flip-flop
- Master/slave J-K flip-flop
- T flip-flop
- T flip-flop with enable